

# ECE 2260 hw04

## 1. Natural Response of a Parallel RLC Circuit

The circuit elements in the circuit in Fig. 1 are  $R = 125\ \Omega$ ,  $L = 200\ \text{mH}$ , and  $C = 5\ \mu\text{F}$ . The initial inductor current is  $-300\ \text{mA}$  and the initial capacitor voltage is  $25\ \text{V}$ .

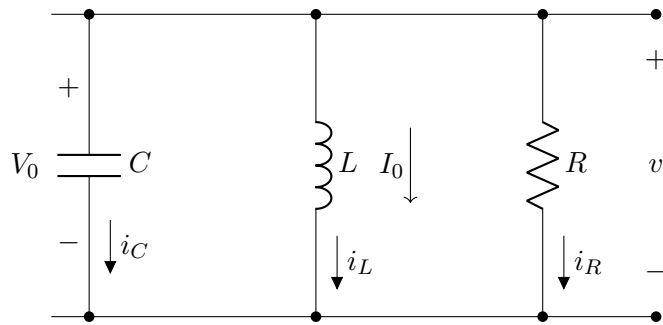


Figure 1: A circuit used to illustrate the natural response of a parallel RLC circuit.

- Calculate the initial current in each branch of the circuit.
- Find  $v(t)$  for  $t \geq 0$ .
- Find  $i_L(t)$  for  $t \geq 0$ .

## 2. Parallel RLC Circuit Response

The resistance, inductance, and capacitance in a parallel  $RLC$  circuit are  $2000\ \Omega$ ,  $250\ \text{mH}$ , and  $10\ \text{nF}$ , respectively.

- a) Calculate the roots of the characteristic equation that describe the voltage response of the circuit.
- b) Will the response be over-, under-, or critically damped?
- c) What value of  $R$  will yield a damped frequency of  $12\ \text{krad s}^{-1}$ ?
- d) What are the roots of the characteristic equation for the value of  $R$  found in (c)?
- e) What value of  $R$  will result in a critically damped response?

### 3. Damping in Parallel RLC Circuits

A parallel, natural response RLC circuit is in its simplest form (a resistor  $R$ , an inductor  $L$ , and capacitor  $C$  all in parallel). Given the following component values, determine if the response is over-damped, under-damped, or critically damped.

(i)  $R = 400\ \Omega$ ,  $L = 25\ \text{mH}$ , and  $C = 25\ \text{nF}$

(ii)  $R = 625\ \Omega$ ,  $L = 25\ \text{mH}$ , and  $C = 25\ \text{nF}$

#### 4. Circuit with Synchronous Switches

The two switches in the circuit seen in Fig. 2 operate synchronously. When switch 1 is in position a, switch 2 is in position d. When switch 1 moves to position b, switch 2 moves to position c. Switch 1 has been in position a for a long time. At  $t = 0$ , the switches move to their alternate positions. Find  $v_o(t)$  for  $t \geq 0$ .

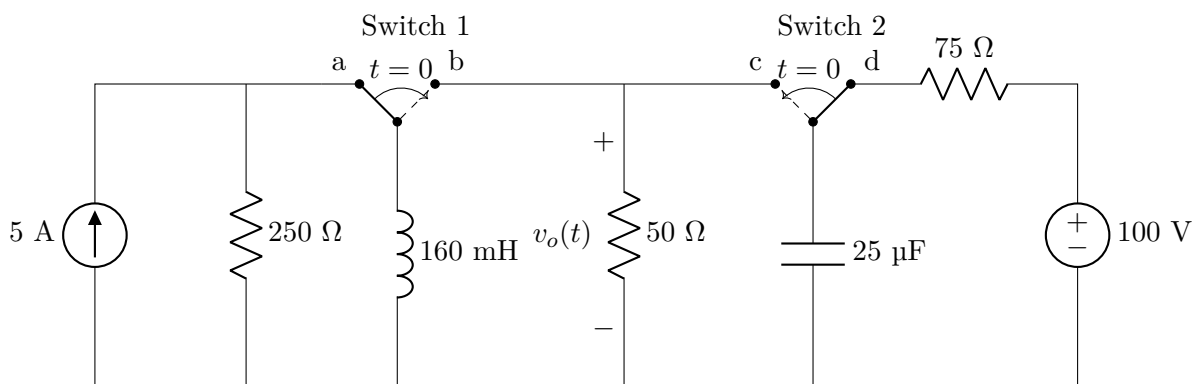


Figure 2: Circuit for problem.

## 5. Circuit with Dependent Source

The switch in the circuit of Fig. 3 has been in position a for a long time. At  $t = 0$  the switch moves instantaneously to position b. Find  $v_o(t)$  for  $t \geq 0$ .

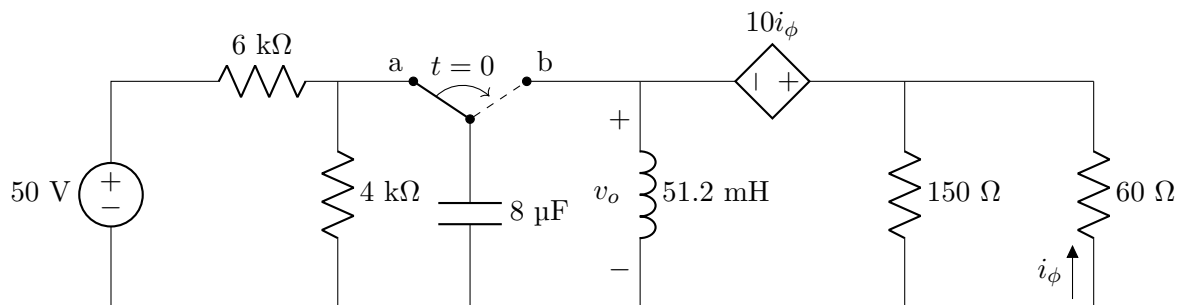


Figure 3: Circuit for problem.

## 6. RLC Step Response

The switch in the circuit in Fig. 4 has been open for a long time before closing at  $t = 0$ . Find  $i_o(t)$ .

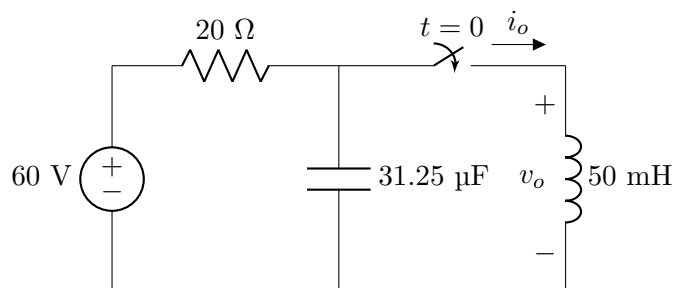


Figure 4: Circuit for problem

## 7. RLC Step Response

The left switch in the circuit in Fig. 5 has been closed for a long time. The right switch has been open for a long time. At time  $t = 0$ , the left switch opens, and the right switch closes simultaneously.

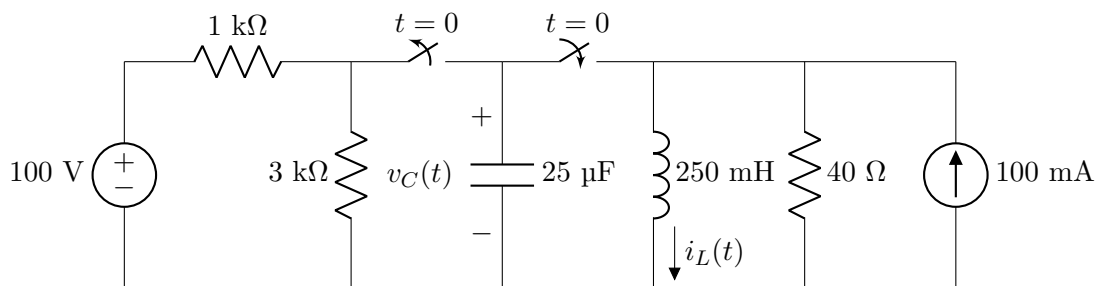


Figure 5: Circuit for problem.

- a)  $i_L(t)$  for  $t \geq 0$ ,
- b) Find  $v_C(t)$ .