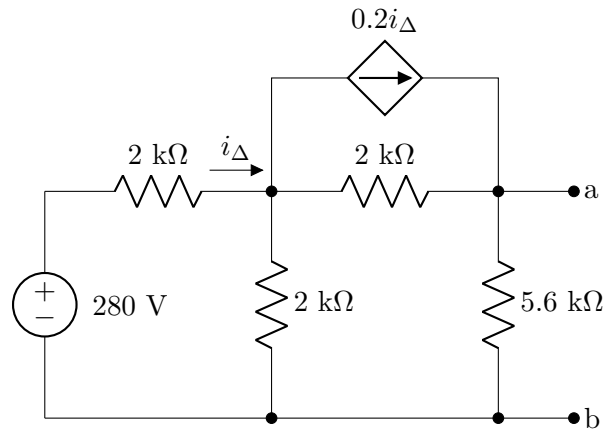


ECE 2260 quiz01

Name: _____ SOLUTIONS

Find the Thevenin equivalent with respect to the terminals a,b for the circuit below. Write your answer in the box provided.



Solution: We begin by finding the Thevenin voltage v_{th} across terminals a and b . We will need to find the voltage over a and b with no load connected. We see there are two nodes and a dependent current source, so we will have a three equation system to solve. Solving this gives us $v_1 = 120$ V, $v_{Th} = 112$ V, and $i_{\Delta} = 80$ mA.

Next, we need to find the Thevenin resistance R_{th} . To do this, we short a and b and solve for the current over the short i_{sc} . Here we will use mesh current with two mesh currents i_{Δ} and i_{sc} . Solving this system gives us $i_{\Delta} = 100$ mA and $i_{sc} = 60$ mA.

Finally, we can find the Thevenin resistance as

$$R_{th} = \frac{v_{th}}{i_{sc}} = \frac{112 \text{ V}}{60 \text{ mA}} = 1.867 \text{ k}\Omega.$$

$$v_{th} = 112 \text{ V}$$

$$R_{th} = 1.867 \text{ k}\Omega$$