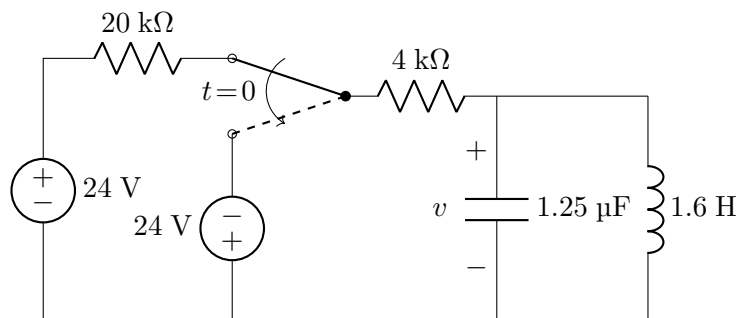


ECE 2260 quiz05

Name: _____ SOLUTIONS

For the following circuit, find $v(t)$.



Solution: First, we should notice that we need to get the circuit in the parallel form with a source transformation after $t \geq 0$. This would give us a current source with a parallel resistor, capacitor, and inductor. The current source value is given by $I_s = V/R = 24 \text{ V}/20 \text{ k}\Omega = 1.2 \text{ mA}$. The parallel resistance is simply $R = 20 \text{ k}\Omega$.

We should figure out some initial conditions. The initial current through the inductor is $i_L(0^-) = \frac{24 \text{ V}}{24 \text{ k}\Omega} = 1 \text{ mA}$. The initial voltage across the capacitor is $v_C(0^-) = 0 \text{ V}$. We can find $i'(0^+) = \frac{v(0^+)}{L} = \frac{0 \text{ V}}{1.6 \text{ H}} = 0 \text{ A/s}$. Lastly, we can find $I_f = \frac{-24 \text{ V}}{4 \text{ k}\Omega} = -6 \text{ mA}$.

We next need to determine the natural response characteristic roots

$$S_{1,2} = -100 \pm j700 \text{ rad/s.}$$

We can then find the natural response

$$i_L(t) = I_f + e^{-100t}(B'_1 \cos(700t) + B'_2 \sin(700t)).$$

We can find B'_1 using the initial condition

$$i_L(0^+) = I_f + B'_1 = 1 \text{ mA} \implies B'_1 = 7 \text{ mA.}$$

We can find B'_2 using the derivative initial condition

$$i'_L(0^+) = -100B'_1 + 700B'_2 = 0 \text{ A/s} \implies B'_2 = 1 \text{ mA.}$$

Putting it together

$$i_L(t) = -6 + e^{-100t}(7 \cos(700t) + \sin(700t)) \text{ mA.}$$

However, we are looking for $v(t)$! We can find $v(t)$ using $v(t) = L \frac{di_L(t)}{dt}$.

$$v(t) = 1.6 \text{ H}(-100e^{-100t}(0.007 \text{ A} \cos(700t) + 0.001 \text{ A} \sin(700t)) + e^{-100t}(-0.007 \text{ A} \cdot 700 \sin(700t) + 0.001 \text{ A} \cdot 700 \cos(700t))) \text{ V} \\ = -8 \text{ V} e^{-100t} \sin(700t)$$

We can also solve this from the voltage side. The characteristic equation is the same, so we can write the voltage as

$$v(t) = e^{-100t}(B_1 \cos(700t) + B_2 \sin(700t))$$

We can find B_1 using the initial condition:

$$v(0^+) = B_1 = 0 \text{ V}$$

We can find B_2 using the derivative initial condition

$$v'(0^+) = \frac{i_c(0^+)}{C} = \frac{-7 \text{ mA}}{1.25 \text{ }\mu\text{F}} = -5600 \text{ V/s} \implies 700B_2 = -5600 \text{ V/s} \implies B_2 = -8 \text{ V}$$

Putting it together

$$v(t) = -8 \text{ V} e^{-100t} \sin(700t) t > 0.$$

Let's give a more complete final answer

$$v(t) = \begin{cases} 0 \text{ V}, & t < 0 \\ -8 \text{ V} e^{-100t} \sin(700t), & t \geq 0 \end{cases}$$

It might be helpful to visualize $v(t)$ with a plot.

