

ECE 2260 hw04

1. Natural Response of a Parallel RLC Circuit

The circuit elements in the circuit in Fig. 1 are $R = 125\ \Omega$, $L = 200\ \text{mH}$, and $C = 5\ \mu\text{F}$. The initial inductor current is $-300\ \text{mA}$ and the initial capacitor voltage is $25\ \text{V}$.

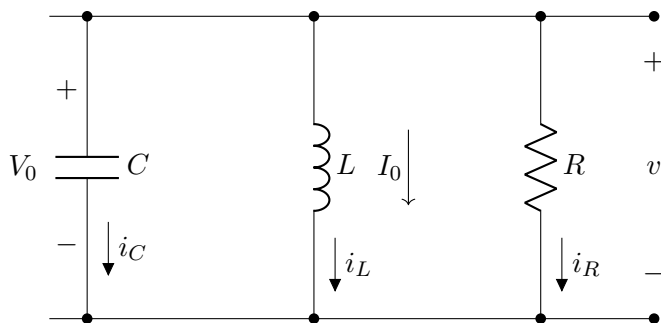


Figure 1: A circuit used to illustrate the natural response of a parallel RLC circuit.

- Calculate the initial current in each branch of the circuit.
- Find $v(t)$ for $t \geq 0$.
- Find $i_L(t)$ for $t \geq 0$.

2. Parallel RLC Circuit Response

The resistance, inductance, and capacitance in a parallel RLC circuit are $2000\ \Omega$, $250\ \text{mH}$, and $10\ \text{nF}$, respectively.

- a) Calculate the roots of the characteristic equation that describe the voltage response of the circuit.
- b) Will the response be over-, under-, or critically damped?
- c) What value of R will yield a damped frequency of $12\ \text{krad s}^{-1}$?
- d) What are the roots of the characteristic equation for the value of R found in (c)?
- e) What value of R will result in a critically damped response?

3. Damping in Parallel RLC Circuits

A parallel, natural response RLC circuit is in its simplest form (a resistor R , an inductor L , and capacitor C all in parallel). Given the following component values, determine if the response is over-damped, under-damped, or critically damped.

(i) $R = 400\ \Omega$, $L = 25\ \text{mH}$, and $C = 25\ \text{nF}$

(ii) $R = 625\ \Omega$, $L = 25\ \text{mH}$, and $C = 25\ \text{nF}$

4. Circuit with Synchronous Switches

The two switches in the circuit seen in Fig. 2 operate synchronously. When switch 1 is in position a, switch 2 is in position d. When switch 1 moves to position b, switch 2 moves to position c. Switch 1 has been in position a for a long time. At $t = 0$, the switches move to their alternate positions. Find $v_o(t)$ for $t \geq 0$.

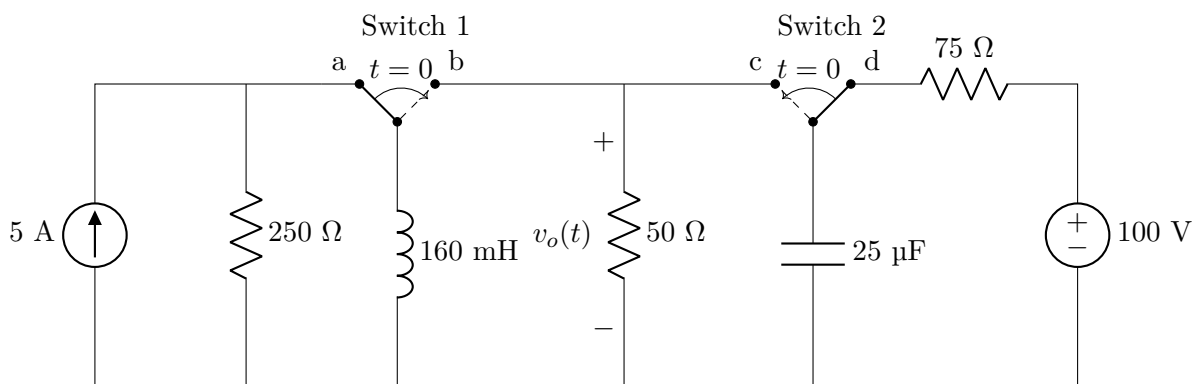


Figure 2: Circuit for problem.

5. Circuit with Dependent Source

The switch in the circuit of Fig. 3 has been in position a for a long time. At $t = 0$ the switch moves instantaneously to position b. Find $v_o(t)$ for $t \geq 0$.

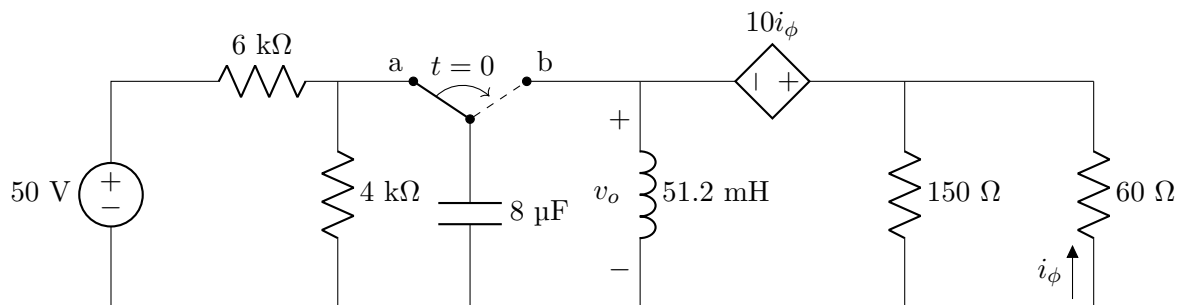


Figure 3: Circuit for problem.

6. RLC Step Response

The left switch in the circuit in Fig. 4 has been closed for a long time. The right switch has been open for a long time. At time $t = 0$, the left switch opens, and the right switch closes simultaneously.

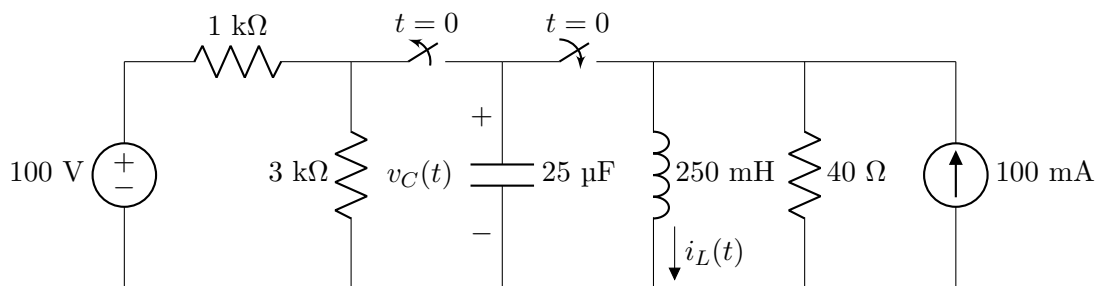


Figure 4: Circuit for problem.

- $i_L(t)$ for $t \geq 0$,
- Find $v_C(t)$.