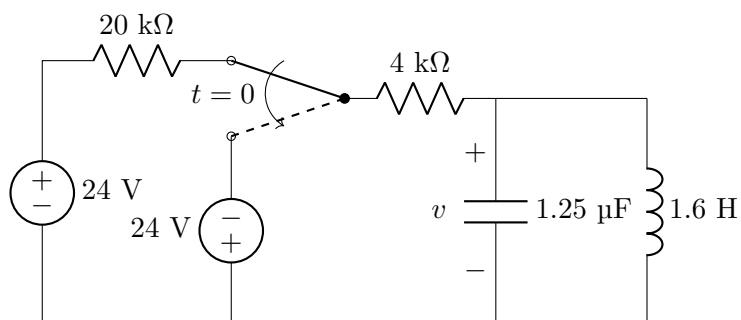


# ECE 2260 hw05

## 1. RLC circuits

For the following circuit, find  $v(t)$  for  $t \geq 0$ .



## 2. Critical Damping in Series RLC

In the circuit in Fig. 1 the switch closes at  $t = 0$ . The resistor is adjusted for critical damping. The initial capacitor voltage is 15 V, and the initial inductor current is 6 mA.

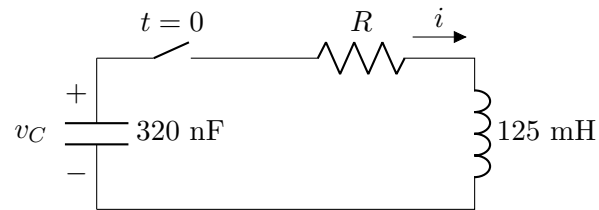


Figure 1: The circuit for problem.

- Find the numerical value of  $R$ .
- Find the numerical values of  $i$  and  $i'(t)$  immediately after the switch is closed.
- Find  $v_C(t)$  for  $t \geq 0$ .

### 3. Step Response of a Series RLC Circuit

The circuit shown in Fig. 2 has been in operation for a long time. At  $t = 0$ , the source voltage suddenly drops to 150 V. Find  $v_o(t)$  for  $t \geq 0$ .

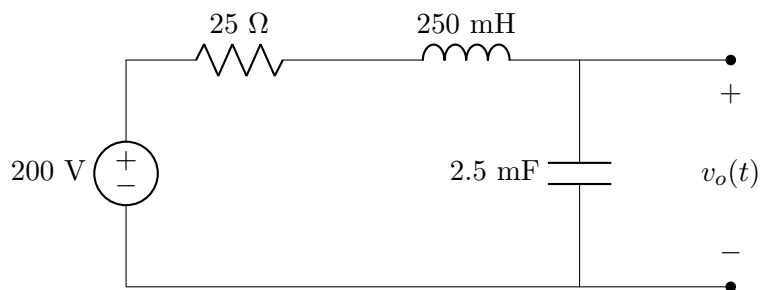


Figure 2: The circuit for problem.

#### 4. Multiple Switches in RLC

The two switches in the circuit seen in Fig. 3 operate synchronously. When switch 1 is in position a, switch 2 is closed. When switch 1 is in position b, switch 2 is open. Switch 1 has been in position a for a long time. At  $t = 0$ , it moves instantaneously to position b. Find  $v_c(t)$ .

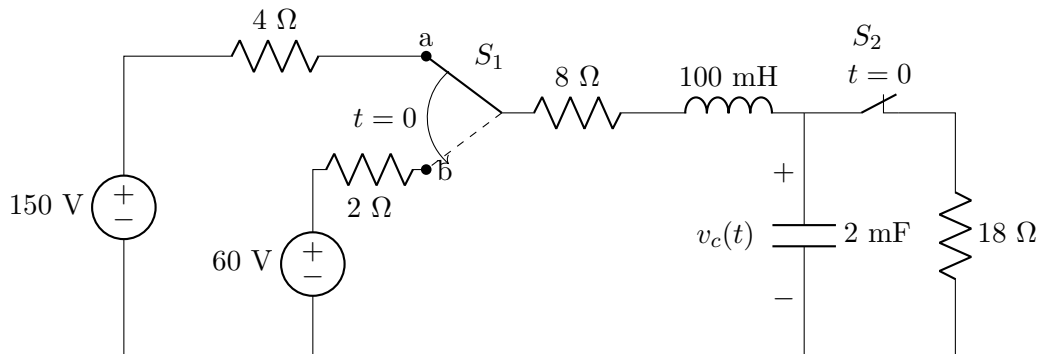


Figure 3: The circuit for problem.

## 5. Step Functions and Window Functions

Step functions can be used to define a *window function*. Thus  $u(t+2) - u(t-3)$  defines a window 1 unit high and 5 units wide located on the time axis between  $-2$  and  $3$ .

A function  $f(t)$  is defined as follows:

$$\begin{array}{ll} f(t) = 0, & t \leq 0 \\ = 5t, & 0 \leq t \leq 10 \text{ s} \\ = -5t + 100, & 10\text{s} \leq t \leq 30 \text{ s} \\ = -50, & 30\text{s} \leq t \leq 40 \text{ s} \\ = 2.5t - 150, & 40\text{s} \leq t \leq 60 \text{ s} \\ = 0, & 60\text{s} \leq t < \infty \end{array}$$

- a) Sketch  $f(t)$  over the interval  $0\text{s} \leq t \leq 60 \text{ s}$ .
- b) Use the concept of the window function to write an expression for  $f(t)$ .

## 6. Step Function Expressions

Use step functions to write the expression for each function shown in Fig. 4.

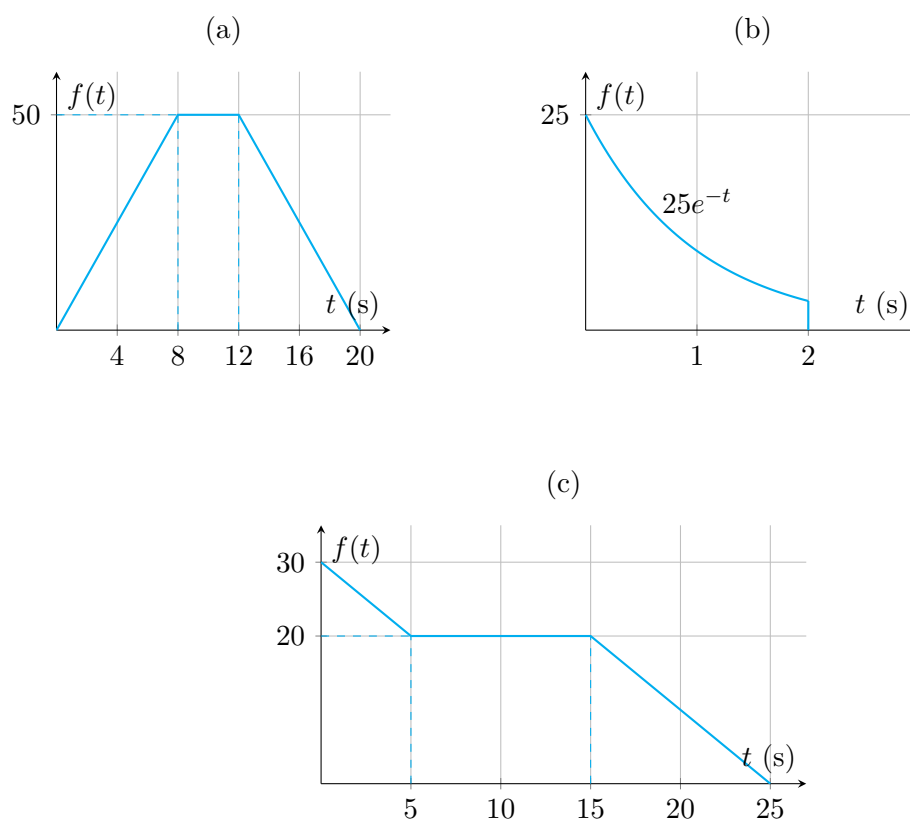


Figure 4: Functions for problem.

## 7. Integrals with Impulses

Evaluate the following integrals:

a)  $I = \int_{-1}^3 (t^3 + 2)[\delta(t) + 8\delta(t - 1)]dt.$

b)  $I = \int_{-2}^2 t^2[\delta(t) + \delta(t + 1.5) + \delta(t - 3)]dt.$