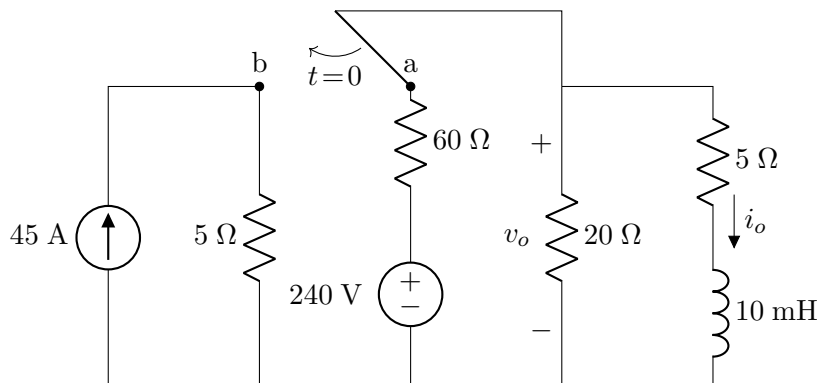


# ECE 2260 quiz03

Name: \_\_\_\_\_ SOLUTIONS

The switch in the circuit below has been in position a for a long time. At  $t=0$ , the switch moves instantaneously to position b.



Find the numerical expressions for  $i_o(t)$  and  $v_o(t)$  for all values of  $t$ .

**Solution:** First, we need to find  $i_o(0^-)$ , which is the current through the inductor just before the switch moves. This is  $i_o(0^-) = 3$  A.

Next, we need to find the Thevenin equivalent circuit seen by the inductor branch after the switch moves to position b at  $t=0$ . This will give us  $V_{th} = 180$  V and  $R_{th} = 9$  Ω. This will give us a time constant  $\tau = \frac{L}{R_{th}} = \frac{10 \text{ mH}}{9 \text{ Ω}} = \frac{1}{900}$  s.

We need the final value of the current  $i_o(\infty) = \frac{V_{th}}{R_{th}} = \frac{180}{9} = 20$  A.

Putting this all together, we can write the expression for  $i_o(t)$

$$i_o(t) = i_o(\infty) + [i_o(0^-) - i_o(\infty)]e^{-t/\tau} = 20 + (3 - 20)e^{-900t} = 20 - 17e^{-900t} \text{ A}, \quad t \geq 0.$$

For all values of  $t$ ,

$$i_o(t) = \begin{cases} 3 \text{ A}, & t < 0, \\ 20 - 17e^{-900t} \text{ A}, & t \geq 0. \end{cases}$$

The voltage  $v_o(t)$  is the voltage across the 20 Ω resistor. However, looking at this, we see this is also the voltage over the 5 Ω resistor, which makes them in parallel with an equivalent resistance of 4 Ω. We know current in this equivalent branch is

$$i_{eq}(t) = 45 \text{ A} - i_o(t) = 45 - (20 - 17e^{-900t}) = 25 + 17e^{-900t} \text{ A}.$$

Therefore, the voltage across this equivalent resistance is

$$v_o(t) = 4 \text{ Ω} i_{eq}(t) = 4(25 + 17e^{-900t}) = 100 + 68e^{-900t} \text{ V}, t \geq 0.$$

Then for all values of  $t$ ,

$$v_o(t) = \begin{cases} 15 \text{ V}, & t < 0, \\ 100 + 68e^{-900t} \text{ V}, & t \geq 0. \end{cases}$$