

# ECE 2260 hw07

## 1. RLC Impedance

A  $200\ \Omega$  resistor is in series with a  $62.5\ \mu\text{F}$  capacitor. This series combination is in parallel with a  $400\ \text{mH}$  inductor.

- a) Express the equivalent  $s$ -domain impedance of these parallel branches as a rational function.
- b) Determine the numerical values of the poles and zeros.

## 2. Poles and Zeros of Impedance

Find the poles and zeros of the impedance seen looking into the terminals a,b of the circuit shown in Fig. 1.

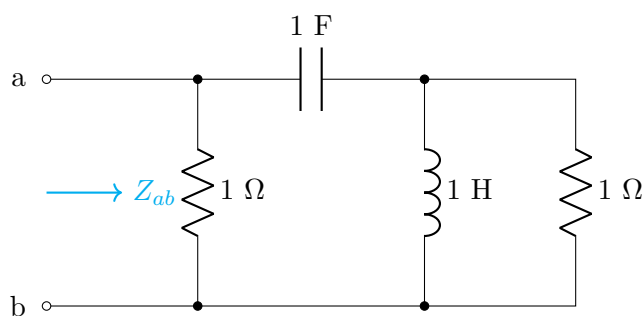


Figure 1: Circuit for problem.

### 3. Step Response of RLC Circuit

Find  $V_o$  and  $v_o$  in the circuit shown in Fig. 2 if the initial energy is zero and the switch is closed at  $t = 0$ .

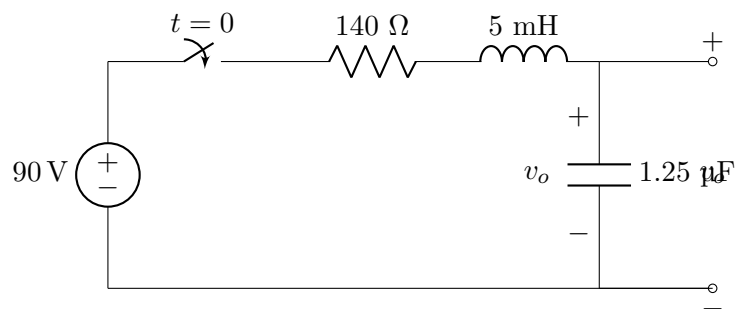


Figure 2: Circuit for Problem P13.9.

#### 4. Switching RLC Circuit Response

The make-before-break switch in the circuit in Fig. 3 has been in position a for a long time. At  $t = 0$ , it moves instantaneously to position b. Find  $v_o$  for  $t \geq 0$ .

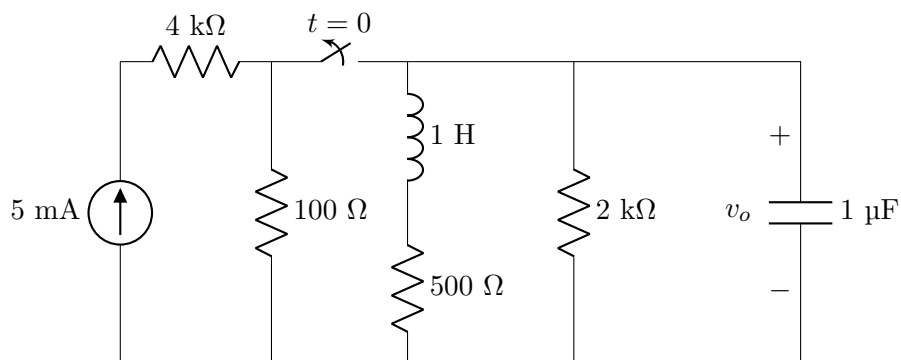


Figure 3: Circuit for problem.

## 5. Circuit Analysis with Laplace Transforms

There is no energy stored in the circuit in Fig. 4 at the time the voltage source is turned on, and  $v_g = 325u(t)$  V.

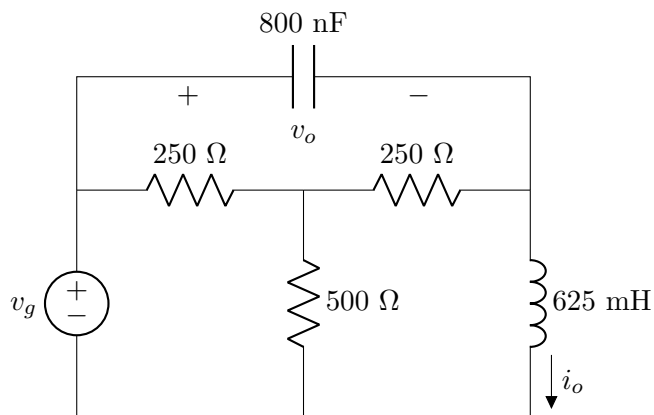


Figure 4: Circuit for problem.

- Find  $V_o$  and  $I_o$ .
- Find  $v_o$  and  $i_o$ .
- Do the solutions for  $v_o$  and  $i_o$  make sense in terms of known circuit behavior? Explain.

## 6. Laplace Transform Circuit Analysis

Find  $v_o$  in the circuit shown in Fig. 5 if  $i_g = 20u(t)$  mA. There is no energy stored in the circuit at  $t = 0$ .

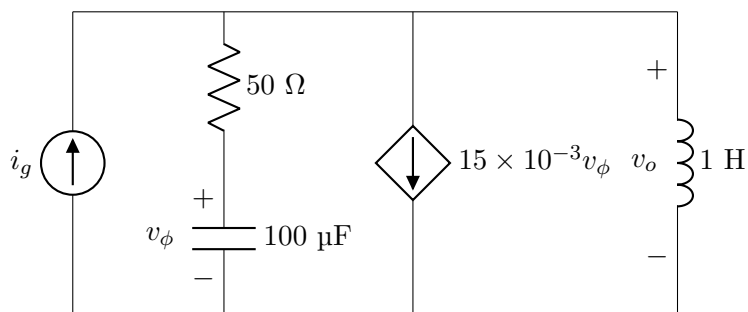


Figure 5: Circuit for problem.