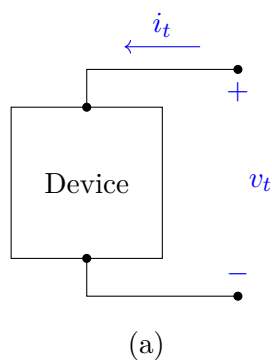


# ECE 2260 hw01

## 1. Basic model

The voltage and current were measured at the terminals of the device shown in Fig. 1 (a). The results are tabulated in Fig. 1 (b).



$v_t$ (V)	$i_t$ (A)
50	0
66	2
82	4
98	6
114	8
130	10

(b)

Figure 1: Device under test

- a) Construct a circuit model for this device using an ideal voltage source in series with a resistor.

**Solution:** Resistor is  $R = 8 \, \Omega$  and voltage source is  $V = 50 \, \text{V}$ .

- b) Use the model to predict the value of  $i_t$  when  $v_t$  is zero.

**Solution:** The model is then

$$v_t = V - i_t R.$$

Setting  $v_t = 0$  gives

$$0 = 50 - i_t(8) \implies i_t = -6.25 \, \text{A}.$$

## 2. Power dissipated in resistor

Find the power dissipated in the  $5\ \Omega$  resistor in the current divider circuit in Fig. 2.

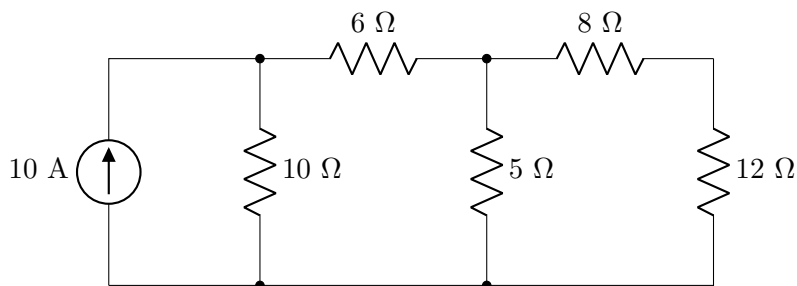


Figure 2: circuit

**Solution:** Using mesh analysis, we have the following mesh equations:

$$\text{Mesh 1: } (i_1 - 10\text{ A}) \cdot 10\ \Omega + (i_1 - i_2) \cdot 6\ \Omega + (i_1 - i_2) \cdot 5\ \Omega = 0\text{ V}$$

$$\text{Mesh 2: } (i_2 - i_1) \cdot 5\ \Omega + i_2 \cdot 20\ \Omega = 0\text{ V.}$$

Rearranging these equations gives:

$$\text{Mesh 1: } i_1(21\ \Omega) + i_2(-5\ \Omega) = 100\text{ V}$$

$$\text{Mesh 2: } i_1(-5\ \Omega) + i_2(25\ \Omega) = 0\text{ V.}$$

Solving these equations simultaneously, we get  $i_1 = 5\text{ A}$  and  $i_2 = 1\text{ A}$ . The current through the resistor is then 4 A. The power dissipated in the  $5\ \Omega$  resistor is then:

$$P = I^2 R = (4\text{ A})^2 \cdot 5\ \Omega = 20\text{ W.}$$

### 3. Specifying resistors in current divider

Specify the resistors in the current divider circuit in Fig. 3 to meet the following design criteria:

$$i_g = 50 \text{ mA}; \quad v_g = 25 \text{ V}; \quad i_1 = 0.6i_2;$$

$$i_3 = 2i_2; \quad \text{and} \quad i_4 = 4i_1.$$

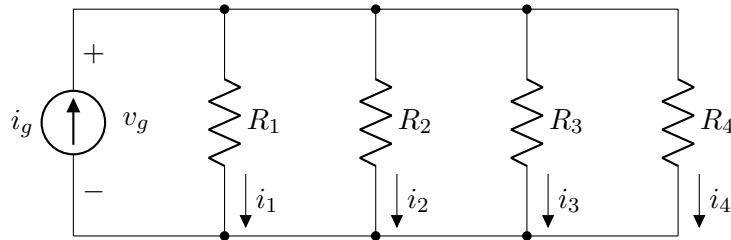


Figure 3: current divider circuit

**Solution:** First, we note that the total current supplied by the current source is the sum of the branch currents:

$$i_g = i_1 + i_2 + i_3 + i_4.$$

Substituting the given relationships between the branch currents, we have:

$$i_g = 0.6i_2 + i_2 + 2i_2 + 4(0.6i_2) = 6 \cdot i_2.$$

Solving for  $i_2$

$$i_2 = \frac{i_g}{6} = \frac{50 \text{ mA}}{6} \approx 8.33 \text{ mA}.$$

Now we can find the other branch currents

$$i_1 = 0.6i_2 = 0.6 \cdot 8.33 \text{ mA} = 5 \text{ mA},$$

$$i_3 = 2i_2 = 2 \cdot 8.33 \text{ mA} = 16.67 \text{ mA},$$

$$i_4 = 4i_1 = 4 \cdot 5 \text{ mA} = 20 \text{ mA}.$$

Next, we can find the voltage across each resistor using Ohm's law. Since all resistors are in parallel, they all have the same voltage drop  $v_g = 25 \text{ V}$ . Now we can calculate each resistor value:

$$R_1 = \frac{v_g}{i_1} = \frac{25 \text{ V}}{5 \text{ mA}} = 5 \text{ k}\Omega,$$

$$R_2 = \frac{v_g}{i_2} = \frac{25 \text{ V}}{8.33 \text{ mA}} = 3 \text{ k}\Omega,$$

$$R_3 = \frac{v_g}{i_3} = \frac{25 \text{ V}}{16.67 \text{ mA}} = 1.5 \text{ k}\Omega,$$

$$R_4 = \frac{v_g}{i_4} = \frac{25 \text{ V}}{20 \text{ mA}} = 1.25 \text{ k}\Omega.$$

#### 4. Node-voltage method power dissipation

Use the node-voltage method to find the total power dissipated in the circuit in Fig. 4.

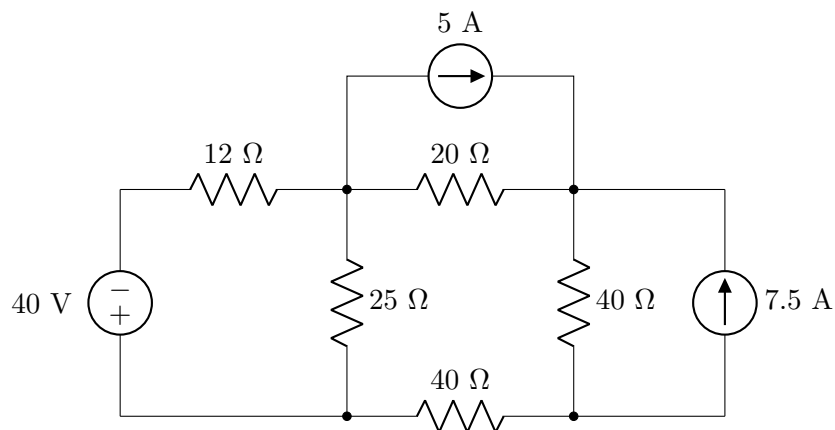


Figure 4: Node voltage circuit

**Solution:** Solving for three nodes (top left: 1, top right: 2, bottom right: 3) using node-voltage method, we have  $v_1 = -10$  V,  $v_2 = 132$  V, and  $v_3 = -84$  V. We can find the power for each element:

$$\begin{aligned} p_{5A} &= -710 \text{ W} \\ p_{7.5A} &= -1620 \text{ W} \\ p_{40V} &= -100 \text{ W} \\ p_{12\Omega} &= 75 \text{ W} \\ p_{25\Omega} &= 4 \text{ W} \\ p_{20\Omega} &= 1008.2 \text{ W} \\ p_{40\Omega,l} &= 176.4 \text{ W} \\ p_{40\Omega,r} &= 1166.4 \text{ W} \end{aligned}$$

The power dissipated in the resistors is then

$$p_{\text{dissipated}} = 75 \text{ W} + 4 \text{ W} + 1008.2 \text{ W} + 176.4 \text{ W} + 1166.4 \text{ W} = 2430 \text{ W}.$$

You can verify that the total power supplied equals the total power dissipated:

$$p_{\text{total}} = -2430 \text{ W} + 2430 \text{ W} = 0 \text{ W}.$$

## 5. Node-voltage method branch currents

Use the node-voltage method to find the branch currents  $i_1$ ,  $i_2$ , and  $i_3$  in the circuit in Fig. 5.

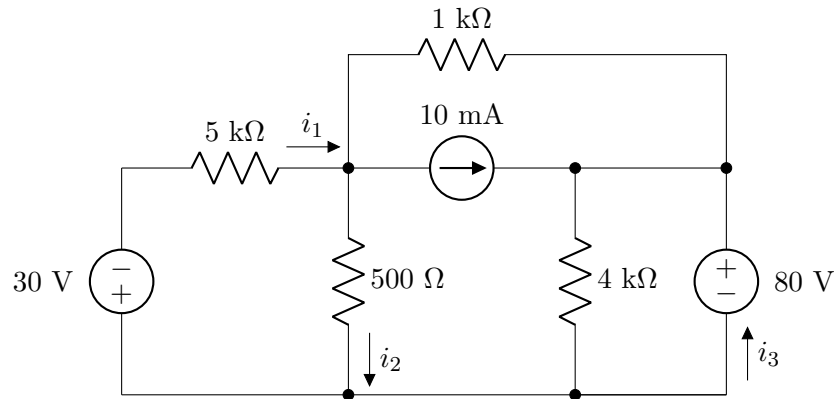


Figure 5: Circuit

**Solution:** We notice there is only one node on the center left. We can write a node-voltage equation for that node (call it  $v_1$ )

$$\frac{v_1 + 30 \text{ V}}{5 \text{ k}\Omega} + \frac{v_1 - 80 \text{ V}}{1 \text{ k}\Omega} + 10 \text{ mA} + \frac{v_1}{500 \Omega} = 0 \text{ A}$$

We can isolate  $v_1$  such that

$$v_1 \left( \frac{1}{5 \text{ k}\Omega} + \frac{1}{1 \text{ k}\Omega} + \frac{1}{500 \Omega} \right) = -10 \text{ mA} + 80 \text{ mA} - 6 \text{ mA}.$$

Solving gives  $v_1 = 20 \text{ V}$ . Using this, we can find each branch current individually. Solving for  $i_1$  is just

$$i_1 = \frac{-30 \text{ V} - 20 \text{ V}}{5 \text{ k}\Omega} = -10 \text{ mA}.$$

Solving for  $i_2$  is

$$i_2 = \frac{20 \text{ V}}{500 \Omega} = 40 \text{ mA}.$$

Lastly, we look at the center-right node and notice that the voltage referenced to a bottom ground is 80 V. Thus, we can solve for  $i_3$  as

$$i_3 = -10 \text{ mA} + \frac{80 \text{ V} - 20 \text{ V}}{1 \text{ k}\Omega} + \frac{80 \text{ V}}{4 \text{ k}\Omega} = 70 \text{ mA}.$$

## 6. DC Thevenin equivalent

Find the Thevenin equivalent with respect to the terminals a,b for the circuit seen in Fig. 6.

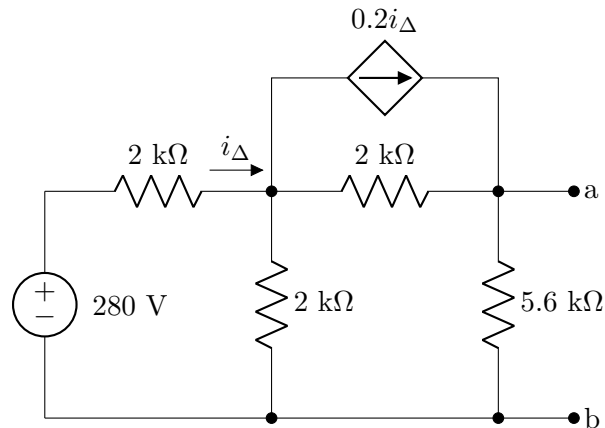


Figure 6: Circuit for Thevenin equivalent problem

**Solution:** We begin by finding the Thevenin voltage  $v_{th}$  across terminals a and b. We will need to find the voltage over a and b with no load connected. We see there are two nodes and a dependent current source, so we will have a three equation system to solve. Solving this gives us  $v_1 = 120$  V,  $v_{Th} = 112$  V, and  $i_{\Delta} = 80$  mA.

Next, we need to find the Thevenin resistance  $R_{th}$ . To do this, we short a and b and solve for the current over the short  $i_{sc}$ . Here we will use mesh current with two mesh currents  $i_{\Delta}$  and  $i_{sc}$ . Solving this system gives us  $i_{\Delta} = 100$  mA and  $i_{sc} = 60$  mA.

Finally, we can find the Thevenin resistance as

$$R_{th} = \frac{v_{th}}{i_{sc}} = \frac{112 \text{ V}}{60 \text{ mA}} = 1.867 \text{ k}\Omega.$$

## 7. AC Thevenin equivalent

Use source transformations to find the Thévenin equivalent circuit with respect to the terminals a,b for the circuit shown in Fig. P9.45.

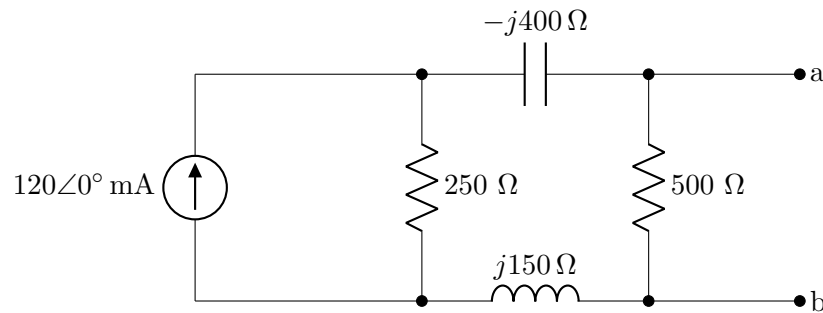


Figure 7: Circuit for AC Thevenin equivalent problem

**Solution:** After a series of source transformations and simplifications, we find the Thévenin equivalent circuit with respect to terminals a and b to be a voltage source of  $V_{th} = (18 + j6) \text{ V}$  with an impedance of  $Z_{th} = (200 - j100) \Omega$ .

## 8. Phasor voltage

Find the phasor voltage  $\mathbf{V}_g$  and phasor current  $\mathbf{I}_g$  in the circuit shown in Fig. 8.

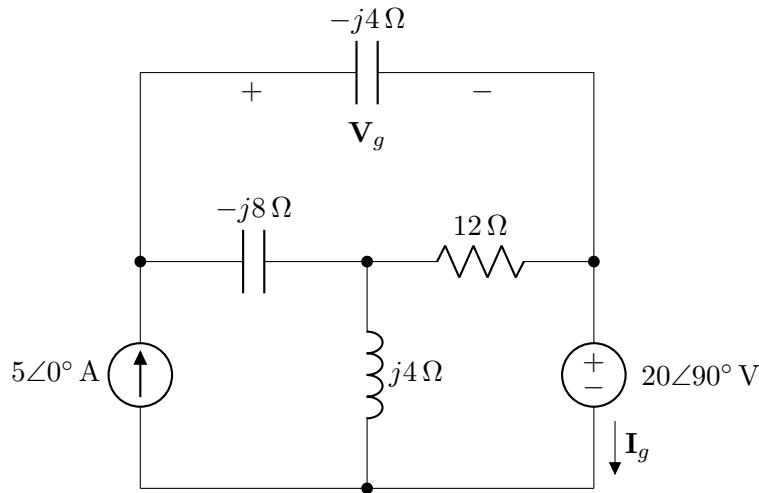


Figure 8: Circuit for phasor voltage problem

**Solution:** We can solve this using either mesh or nodal analysis. Here, we will use mesh analysis. We define mesh currents as shown in Fig. 8.

$$\text{Mesh 1: } I_1(-j4 \, \Omega) + (I_1 - I_g)(12 \, \Omega) + (I_1 - 5 \, \text{A})(-j8 \, \Omega) = 0 \, \text{V}$$

$$\text{Mesh 2: } (I_g - 5 \, \text{A})(j4 \, \Omega) + (I_g - I_1)(12 \, \Omega) + j20 \, \text{V} = 0 \, \text{V}$$

Rearranging, we have

$$((12 - j12) \, \Omega) I_1 + (-12) I_g = -j40 \, \text{V}$$

$$(-12) I_1 + ((12 + j4) \, \Omega) I_g = 0 \, \text{V}$$

Solving this system of equations, we get  $\mathbf{I}_1 = (4.667 - j0.667) \, \text{A}$  and  $\mathbf{I}_g = (4 - j2) \, \text{A}$ . To find  $\mathbf{V}_g$ , we can use

$$\mathbf{V}_g = \mathbf{I}_1 - j4 \, \Omega = (-2.667 - j18.667) \, \text{V}.$$



## 9. AC power transfer

The load impedance  $Z_L$  for the circuit shown in Fig. 9 is adjusted until maximum average power is delivered to  $Z_L$ . What is the impedance  $Z_L$  in ohms?

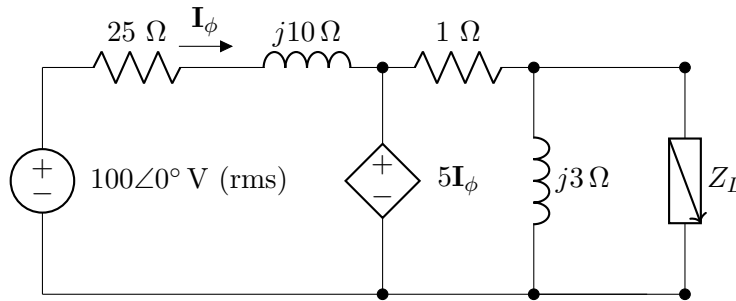


Figure 9: Circuit for AC power transfer problem

**Solution:** The average power delivered will be maximized when  $Z_L$  is the complex conjugate of the Thevenin impedance seen from the load terminals. We can start by finding the open circuit voltage at the terminals where  $Z_L$  is connected. To do this, we first need to find the current  $I_\phi$  supplied by the voltage source. We can first do a voltage loop on the left-hand side of the circuit

$$-100 \text{ V} - I_\phi(25 + j10) \Omega + 5I_\phi = 0.$$

We can solve for  $I_\phi = (-4 + j2) \text{ A}$ . Now we can find the voltage over the dependent source and use a voltage divider to find the open circuit voltage  $V_{Th}$

$$V_{Th} = 5I_\phi \cdot \frac{j3 \Omega}{(1 + j3) \Omega} = (-21 + j3) \text{ V}.$$

Next we can short the load terminals and find the short circuit current  $I_{SC}$ . We can use mesh analysis to find the current through the short. Notice this doesn't impact  $I_\phi$  since it is on the left side of the circuit. We notice that the voltage supplied by the dependent source is also unaffected, so we can simply find  $I_{SC}$  by

$$I_{SC} = \frac{5I_\phi}{1 \Omega} = (-20 + j10) \text{ A}.$$

Now we can find the Thevenin impedance

$$Z_{Th} = \frac{V_{Th}}{I_{SC}} = (0.9 + j0.3) \Omega.$$

Finally, we can find the load impedance for maximum power transfer by taking the complex conjugate

$$Z_L = Z_{Th}^* = (0.9 - j0.3) \Omega.$$

## 10. AC Thevenin equivalent

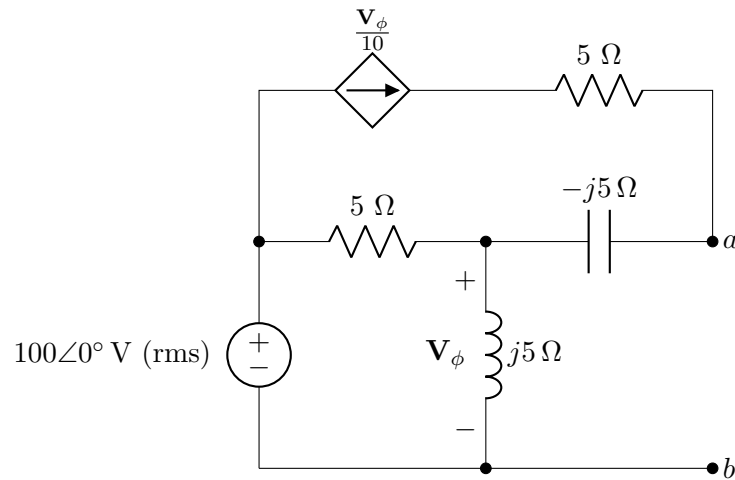


Figure 10: Circuit for AC for Thevenin equivalent problem

**Solution:** To find the Thevenin voltage, we can use the node at the center of the circuit. The nodal analysis equation at this node is

$$\frac{V_\phi}{j5 \, \Omega} + \frac{V_\phi - 100}{5 \, \Omega} - \frac{V_\phi}{10} = 0 \, \text{A}.$$

We can solve  $V_\phi = (40 + j80) \, \text{V}$ . To get the Thevenin voltage, we can use

$$V_{\text{Th}} = V_\phi + (0.1V_\phi)(-j5 \, \Omega) = (80 + j60) \, \text{V}.$$

To solve for the Thevenin impedance, we can short between  $a$  and  $b$  to solve for  $I_{\text{sc}}$ . Using nodal analysis again, we have

$$\frac{V_\phi - 100 \, \text{V}}{5 \, \Omega} + \frac{V_\phi}{j5 \, \Omega} + \frac{V_\phi}{-j5 \, \Omega} = 0 \, \text{A}.$$

Solving, we find  $V_\phi = 100 \, \text{V}$ . Solving for the short-circuit current, we have

$$I_{\text{sc}} = \frac{V_\phi}{-j5 \, \Omega} + \frac{V_\phi}{10} = (10 + j20) \, \text{A}.$$

Finally, we can find the Thevenin impedance as

$$Z_{\text{Th}} = \frac{V_{\text{Th}}}{I_{\text{sc}}} = \frac{(80 + j60) \, \text{V}}{(10 + j20) \, \text{A}} = (4 - j2) \, \Omega.$$