

# ECE 2260 hw03

## 1. Natural Response of an RL Circuit with a Switch

The switch in the circuit shown in Fig. 1 has been in position a for a long time before moving to position b at  $t = 0$ .

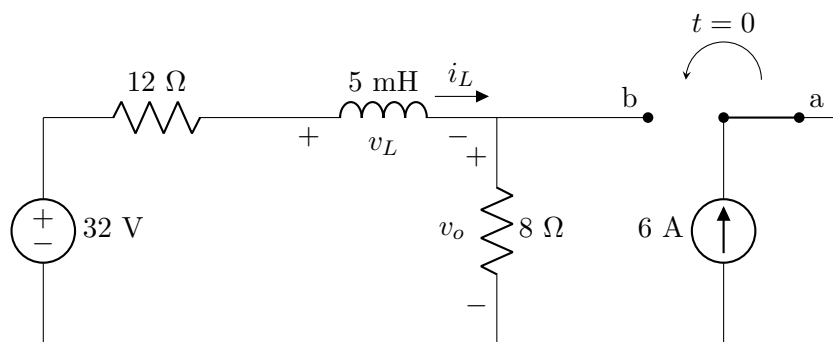


Figure 1: Circuit for problem.

- Find the numerical expressions for  $i_L(t)$  and  $v_o(t)$  for  $t \geq 0$ .
- Find the numerical values of  $v_L(0^+)$  and  $v_o(0^+)$ .

## 2. Step Response of an RL Circuit

The switch in the circuit shown in Fig. 2 has been in position a for a long time. At  $t = 0$ , the switch moves instantaneously to position b.

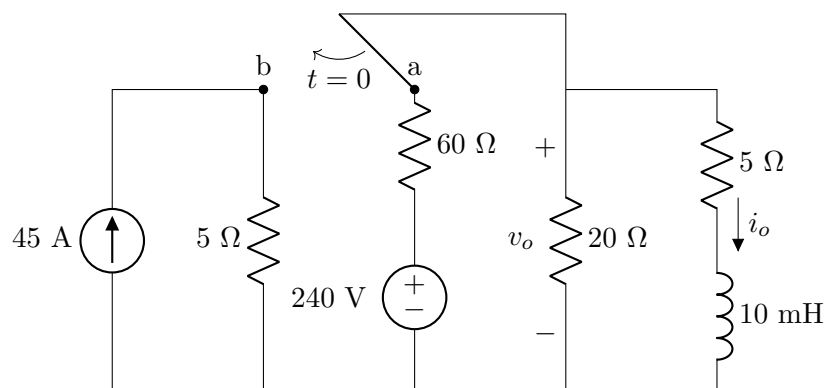


Figure 2: Circuit for step response problem.

- Find the numerical expression for  $i_o(t)$  when  $t \geq 0$ .
- Find the numerical expression for  $v_o(t)$  for  $t \geq 0^+$ .
- Now assume that the switch has been in position b for a long time before moving to position a at  $t = 0$ . Repeat parts (a) and (b).

### 3. Step Response with Dependent Source

The switch in the circuit in Fig. 3 has been open a long time before closing at  $t = 0$ . Find  $i_o(t)$  for  $t \geq 0$ .

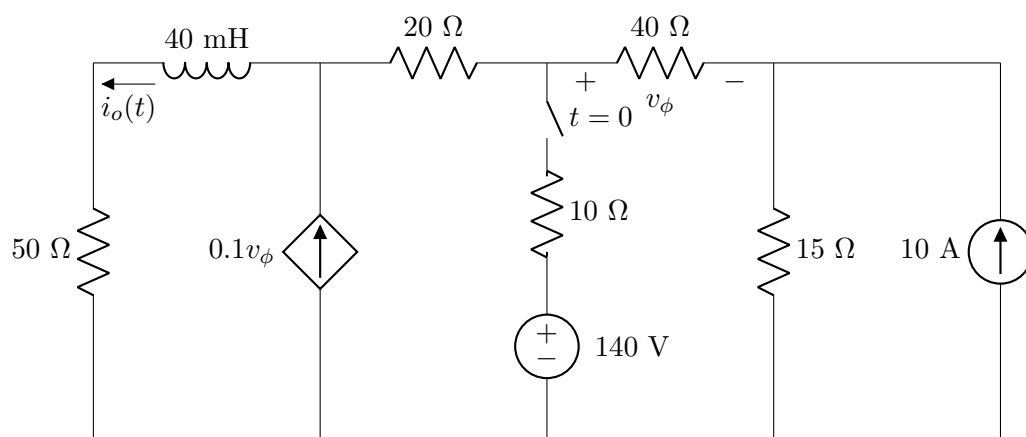


Figure 3: Circuit for problem.

#### 4. Step Response of an RL Circuit with Multiple Sources

The switch in the circuit in Fig. 4 has been open a long time before closing at  $t = 0$ . Find  $v_o(t)$  for  $t \geq 0^+$ .

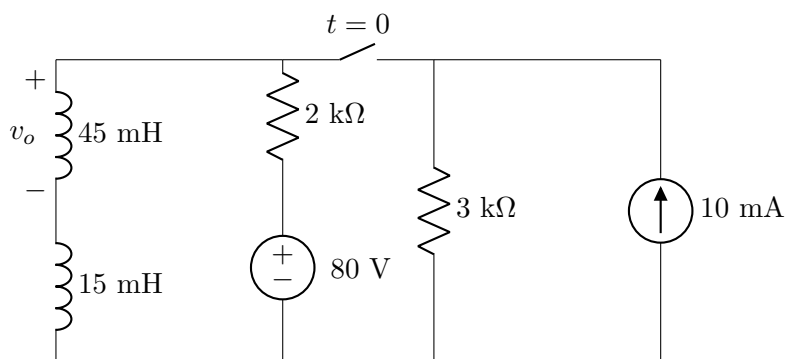


Figure 4: Circuit for problem.

## 5. RC Circuit with Switch and Multiple Sources

Assume that the switch in the circuit of Fig. 5 has been in position a for a long time and that at  $t = 0$  it is moved to position b.

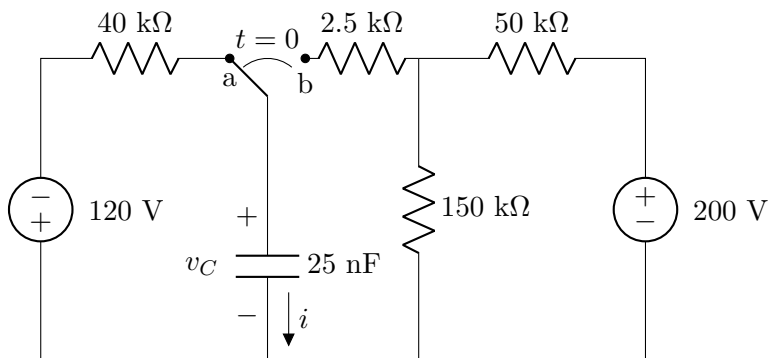


Figure 5: Circuit for problem.

- a) Find  $v_C(t)$  where  $t \geq 0$ .
- b) Next find the expression for  $i(t)$  where  $t \geq 0^+$ .

## 6. Step Response with Dependent Voltage Source

The switch in the circuit shown in Fig. 6 has been in the OFF position for a long time. At  $t = 0$ , the switch moves instantaneously to the ON position. Find  $v_o(t)$  for  $t \geq 0$ .

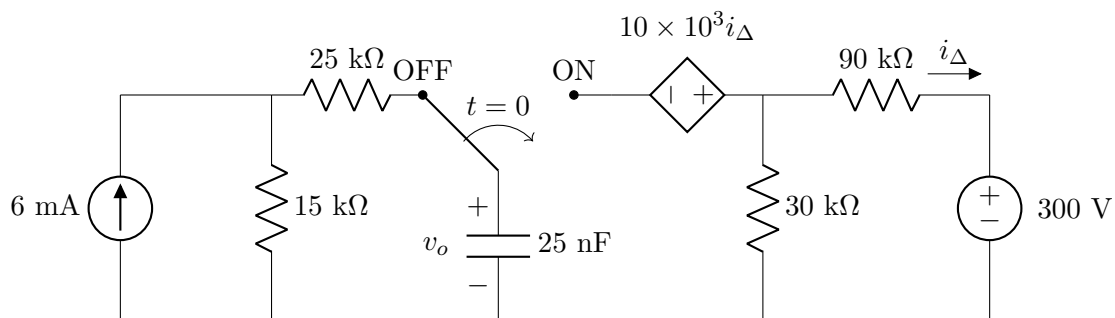


Figure 6: Circuit for problem.

## 7. Sequential Switching in RL Circuit

The action of the two switches in the circuit seen in Fig. 7 is as follows. For  $t < 0$ , switch 1 is in position a and switch 2 is open. This state has existed for a long time. At  $t = 0$ , switch 1 moves instantaneously from position a to position b, while switch 2 remains open. Ten milliseconds after switch 1 operates, switch 2 closes, remains closed for 10 ms and then opens. Find  $v_o(t)$  25 ms after switch 1 moves to position b.

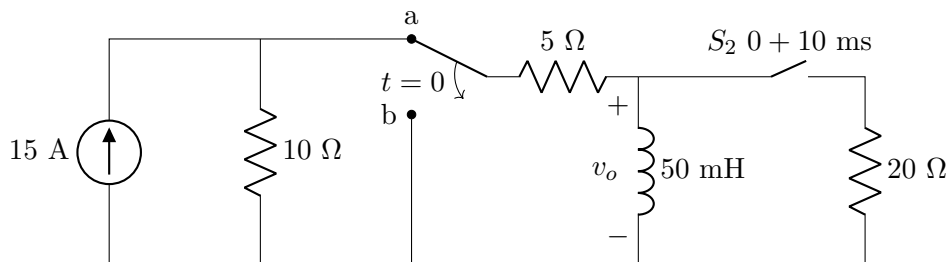


Figure 7: Circuit for problem.

## 8. Sequential Switching with Capacitor

There is no energy stored in the capacitor (i.e., both switches are open) in the circuit in Fig. 8 when switch 1 closes at  $t = 0$ . Switch 2 closes 2.5 ms later. Find  $v_o(t)$  for  $t \geq 0$ .

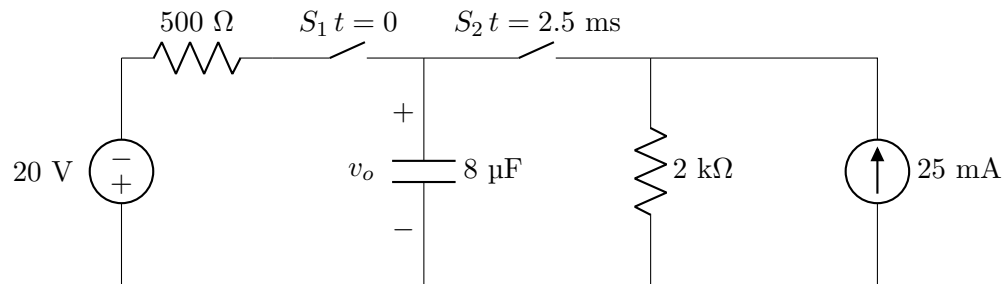


Figure 8: Circuit for problem.



## 9. Unstable RL Circuit with Dependent Source

The inductor current in the circuit in Fig. 9 is 25 mA at the instant the switch is opened. The inductor will malfunction whenever the magnitude of the inductor current equals or exceeds 5 A. How long after the switch is opened does the inductor malfunction?

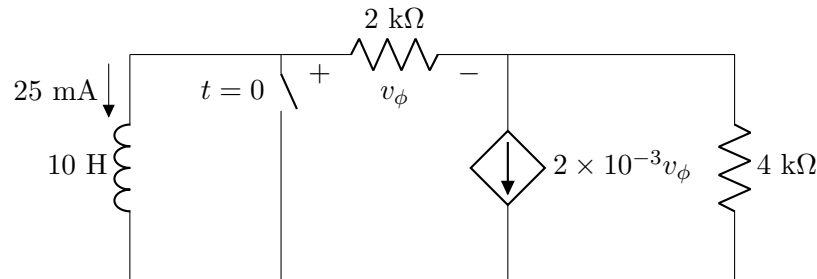


Figure 9: Circuit for problem.