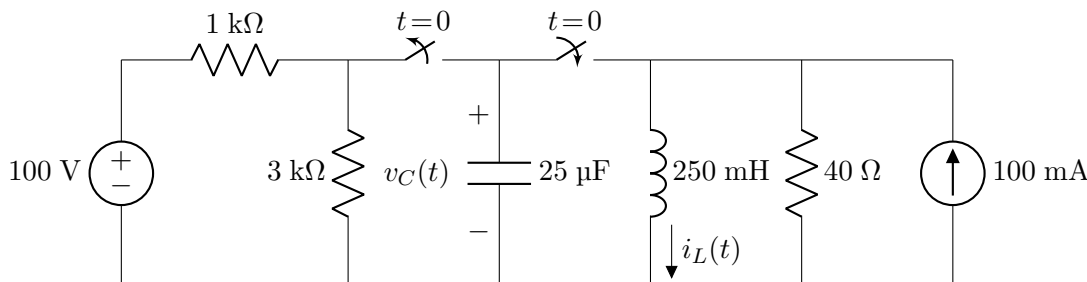


ECE 2260 quiz04

Name: _____ SOLUTIONS

The left switch in the circuit below has been closed for a long time. The right switch has been open for a long time. At time $t=0$, the left switch opens, and the right switch closes simultaneously. Find an expression for $i_L(t)$.



Solution: First, we need to find the initial voltage over the capacitor. This is a voltage divider

$$v_C(0^-) = v_C(0^+) = \frac{3 \text{ k}\Omega}{1 \text{ k}\Omega + 3 \text{ k}\Omega} \cdot 100 \text{ V} = 75 \text{ V}.$$

We can also find the initial current through the inductor. The current source forces 100 mA through the right side of the circuit, so

$$i_L(0^-) = i_L(0^+) = 100 \text{ mA}.$$

We can also find the characteristic roots of the circuit. We see that $\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 40 \cdot 25 \times 10^{-6}} = 500 \text{ s}^{-1}$, and $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{250 \times 10^{-3} \cdot 25 \times 10^{-6}}} = 400 \text{ s}^{-1}$. Since $\alpha > \omega_0$, we have an over-damped circuit. The roots are

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -500 \pm \sqrt{500^2 - 400^2} = -500 \pm 300,$$

so $s_1 = -200$ and $s_2 = -800$. Thus, the response is

$$i_{L,n}(t) = I_f + A_1 e^{-200t} + A_2 e^{-800t}.$$

The final current through the inductor is simply the current source value, so $I_f = 100 \text{ mA}$. To find A_1 and A_2 , we use the initial conditions. At $t=0$,

$$i_L(0) = I_f + A_1 + A_2 = 100 \text{ mA} + A_1 + A_2 = 100 \text{ mA},$$

so $A_1 + A_2 = 0$. We also know that $v_L(t) = v_C(t)$ and that $v_L(t) = L \frac{di_L(t)}{dt}$. We can say that $\frac{di_L(t)}{dt} = \frac{v_L(t)}{L}$. At $t=0$ this would be $i'_L(0^+) = \frac{v_C(0^+)}{L} = 300 \text{ As}^{-1}$. Thus, we see that $i'_L(t) = -200A_1 e^{-200t} - 800A_2 e^{-800t}$, and at $t=0$,

$$i'_L(0) = -200A_1 - 800A_2 = 300 \text{ As}^{-1}.$$

We now have two equations and two unknowns:

$$A_1 + A_2 = 0,$$

$$-200A_1 - 800A_2 = 300 \text{ As}^{-1}.$$

Solving, we find that $A_1 = 500 \text{ mA}$ and $A_2 = -500 \text{ mA}$. Thus, the final expression for $i_L(t)$ is

$$i_L(t) = \begin{cases} 100 \text{ mA}, & t < 0 \\ 100 + 500e^{-200t} - 500e^{-800t} \text{ mA}, & t \geq 0 \end{cases}.$$

We know that the current through the inductor cannot change instantaneously, so $i_L(0^-) = i_L(0^+) = 100 \text{ mA}$, which is confirmed by our expression.